Bs/PHYM-201

2025


(FYUGP)

(2nd Semester)

PHYSICS

(MINOR)

Paper: PHYM-201

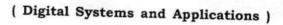

Full Marks: 75

Pass Marks: 40%

Time: 3 hours

(PART : B—DESCRIPTIVE)

(Marks: 50)

The figures in the margin indicate full marks for the questions

Answer five question, taking one from each Group

GROUP-A

- 1. (a) With the help of block diagram, explain the working of CRO.
 - (b) Write a note on classification of ICs. 4

L25/399a

(Turn Over)

c	5	
3		
+		
C)	

 $2 \times 2 = 4$

GROUP-B

- State and prove Boolean laws. *(a)* ю :
- ø of function Describe the demultiplexer. (q)
- 2 Discuss full subtractor with circuit diagram. *(a)* 4
- Find the 1's complement and 2's complement of (10101). (q)

GROUP-C

- Explain a clocked R-S flip-flop with circuit diagram. (a) ı,
- Write a short note on race around conditions. (q)
- 5 J-K master-slave on Write a note flip-flop. (a) ø.
- Draw a block diagram of IC555. (q)

L25/399a

5

(Continued)

Bs/PHYM-201

GROUP-D

- Explain the operation of SISO register with circuit diagram. (a)7.
- 3-byte Jo applications Give some instructions. (q)
- 2 Discuss the working of decade counter. (a)8
- Describe the circuit and function asynchronous counter. (q)

S

GROUP-E

Give an account of input/output devices of a computer. *(a)* 6

9

- partitioning and address decoding. address on Write a note (q)
- Classify the various addressing modes of 8085. *(a)* 10.
- 2 What are the various types of interrupts in 8085? Explain them. (q)

Subject Code : Bs/PHYM-201	Booklet No. A 40				
	Date Stamp				
To be filled in by the Candidate					
BA / BSc / BCom / BBA / BCA 2nd Semester End Term Examination, 2025 (FYUGP) Subject					
Paper	To be filled in by the Candidate				
INSTRUCTIONS TO CANDIDATES	BA / BSc / BCom / BBA / BCA				
The Booklet No. of this script should be quoted in the answer script meant for descriptive type questions and vice versa.	2nd Semester End Term Examination, 2025 (FYUGP)				
2. This paper should be ANSWERED FIRST and submitted within 1 (one) Hour of the commencement of the Examination.	Roll No				

Signature of Scrutiniser(s)

only.

Signature of Examiner(s)

3. While answering the questions of this

booklet, any cutting, erasing, overwriting or furnishing more than one

answer is prohibited. Any rough work, if required, should be done only on the main Answer Book. Instructions

given in each question should be followed for answering that question

Signature of Invigilator(s)

Booklet No. B

Subject

Paper

DESCRIPTIVE TYPE

		25 UGP)	
	(2nd Se	emester)	
	РНҮ	SICS	
	(MII	NOR)	
	Paper : F	PHYM-201	
	(Digital Systems	and Applic	eations)
	(PART : A-	-OBJECTIVE)
	(Mark	s:25)	
The figu	ıres in the margin indic	cate full mar	ks for the questions
	SECT	ion—I	
	(Mark	s:15)	
	ick (✓) mark against s provided :	the correct	answer in the 1×15=15
1. Wh	ich component of CRO O?	is referred	to as 'heart' of
(a)	Time-base generator	()	
(b)	Cathode-ray tube	()	
(c)	Triggering circuit	()	
(d)	Deflection plates	()	
/399			

2.		conductin on of catho	_				side of	conica	
	(a)	graticule	()					
	(b)	aquadag	()					
	(c)	astigmatis	m	()				
	(d)	grid	()						
3.	A k	ilobyte, als	o refe	erred	to as	s KB, is	equal	to	
	(a)	1000 byte	S	()				
	(b)	1024 byte	S	()				
	(c)	2048 byte	S	()				
	(d)	512 bytes		()				
4.	Acc	ording to E	Boolea	ın lav	w, A-	+1=?			
	(a)	1 ()						
	(b)	A ()						
	(c)	0 ()						
	(d)	Α' ()						

5. Which of the following methods is used to minimize Boolean expressions?
(a) Fourier transform ()
(b) Gray code ()
(c) Karnaugh mapping ()
(d) None of the above ()
6. The word 'demultiplex' means
(a) one into many ()
(b) many into one ()
(c) Both of the above ()
(d) None of the above ()
7. Adding 1001 and 0010 gives an output of
(a) 1111 ()
(b) 0000 ()
(c) 1011 ()
(d) 1010 ()

Bs/PHYM-201**/399**

8. The flip-flop is only activated by
(a) positive edge trigger ()
(b) negative edge trigger ()
(c) either positive or negative edge trigger ()
(d) All of the above ()
9. How many states does a decimal counter have?
(a) 5 ()
(b) 10 ()
(c) 15 ()
(d) 0 ()
10. Johnson counter is also known as
(a) asynchronous counter ()
(b) twisted ring counter ()
(c) decade counter ()
(d) register ()

11	. The	e parallel ou	tputs	of a	cou	nter	circuit	represen	t
		*						•	
	(a)	clock coun	t	()				
	(b)	clock frequ	ency		()			
	(c)	clock modu	ılars		()			
	(d)	synchronou	ıs cou	nter		()		
12.	The is c	process of c alled	opyinę	g dat	ta fro	m a	memor	y location	1
	(a)	reading	()					
	(b)	writing	()					
	(c)	controlling	()					
	(d)	booting	()					
Bs/Pi	НҮМ-	201 /399							
		12							

13.	The	list of instructions used by a computer is called
	(a)	program ()
	(b)	CPU ()
	(c)	text ()
	(d)	output ()
14.	Whi	ch of the following memories is volatile?
	(a)	RAM ()
	(b)	ROM ()
	(c)	EPROM ()
	(d)	PROM ()
15.	Clo	ck speed is also known as
	(a)	clock rate ()
	(b)	clock length ()
	(c)	clock set ()
	(d)	clock type ()

Bs/PHYM-201**/399**

SECTION—II

(Marks : 10)

Answer any five of the following questions in brief: 2×5=10

1. Why is electron gun called so?

2. What is VLSI?

3. Give the difference between minterms and maxterms.

4. Give two practical applications of seven-segment display.

5. What do you mean by propagation delay?

6. Why is IC555 timer named 555?

7. What do you mean by universal shift register?

8. How is a ring counter superior to ripple and synchronous counters?

9. What is non-volatile memory?

10. What is meant by a bus?

* * *